



Register Number:

DATE: 24-11-2020

**ST. JOSEPH'S COLLEGE (AUTONOMOUS), BANGALORE-27**  
**B.Sc. ELECTRONICS- III SEMESTER**  
**SEMESTER EXAMINATION: NOVEMBER/DECEMBER 2020**  
**EL 318 DIGITAL ELECTRONICS**

**Time- 2 ½ hrs**

**Max Marks-70**

**This paper contains TWO printed pages and THREE parts**  
**PART-A**

Answer any **FIVE** questions.

5×8=40

- 1 a) With the help of examples explain the weighted and non weighted codes.  
b) What is Gray code? Outline the procedure for converting a given binary number to its Gray code equivalent and a given Gray code to its binary equivalent (4+4)
- 2 a) Draw the circuit diagram of a two input NOR gate using diodes, transistor and resistors. Explain its operation with truth table.  
b) State and prove De Morgan's theorem using truth table. (4+4)
- 3 a) State and explain the Duality theorem.  
b) Draw three continuous negative ideal pulses and describe duty cycle.  
c) With the help of a diagram explain current sourcing & sinking in a standard TTL NAND gate. (2+2+4)
- 4 a) Draw the two input TTL NAND gate and explain its operation. What is the significance of Totem - pole configuration.  
b) Discuss any four parameters of TTL device. (4+4)
- 5 a) Write the truth table for FULL Subtractor. Show how a FULL Subtractor can be constructed using 2 Half Subtractors and a OR gate.  
b) Construct 8:1 Multiplexer and describe it's working. Mention the need for strobe line. (4+4)
- 6 a) What is an encoder? Draw the logic diagram of a decimal to BCD encoder and write its truth table. What is priority encoder?  
b) Write the logic diagram of a BCD to SEVEN segment decoder using IC 7446, along with the functional table. (4+4)
- 7 a) Explain CLEAR and PRESET functions using a truth table for a JK flip flop.  
b) Draw the circuit for a SIPO shift register and explain its working its working for a given data D=1011. (4+4)

**PART-B**

Answer any **FIVE** questions.

5×4=20

- 8 a) Subtract  $(76)_8$  from  $(125)_8$  using 2' s complement.  
b) Add  $(34)_{10}$  and  $(19)_{10}$  in BCD. (2+2)
9. Expand the following SOP expression to minterm and maxterm.


$$A + B\bar{C} + A\bar{B}\bar{D} + ABCD$$

10. Using K maps simplify the expression and draw its equivalent logic gate.


$$F(A,B,C,D) = \sum m (1,3,5,7,8,9,12,13) \text{ and } F(A,B,C,D) = \sum d (2,6,14).$$

11 a) Determine the fan-out when 74XX drives 74LSXX.


(2+2)

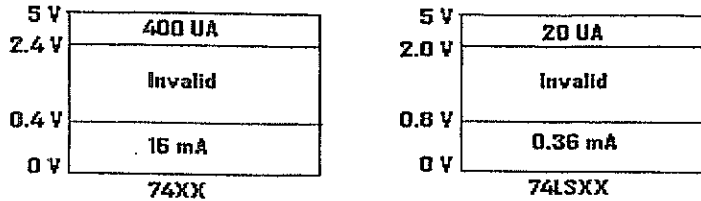

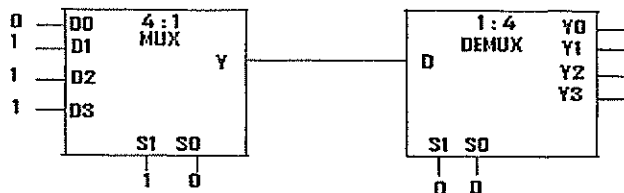- b) The propagation delay time for a gate is 10 ns and power dissipation of 2mW. If 6 such gates are connected in series, what is the total time delay and power dissipation of the circuit.
12. What will be the outputs at Y and Y<sub>0</sub>, Y<sub>1</sub>, Y<sub>2</sub> and Y<sub>3</sub>.



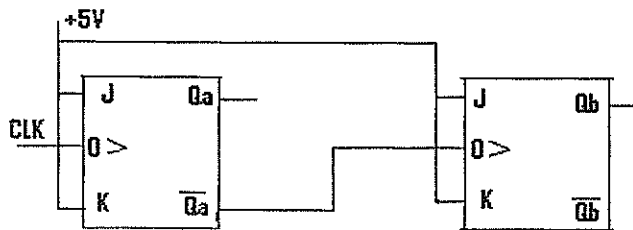13. Draw the output waveforms at Qa and Qb for four clock pulses.



14. Construct an Asynchronous Mod-12 counter and draw the timing diagram.

### PART- C

Answer any FIVE questions.

5×2=10

15. Why Gray code belongs to a class of minimum change code.
16. Which is the fastest logic family? What is the disadvantage of the same.
17. Write the algebraic terms of a 4 -variable expression having a Maxterm M<sub>3</sub> and M<sub>9</sub>.
18. A De multiplexer can switch from 64 data input to its one output line, how many selections lines are required ? Explain.
19. Realize a Half subtractor using basic gates.
20. Mention how RS flip flop can be converted to D flip flop.
- 21 Distinguish between Jonson and Ring counter.

-----END-----